

Assignment 2

[提交作业](#)

截止时间 星期日, 23:59 之前 **得分** 100 **提交** 一份上传文件 **文件类型** pdf

Suppose that you have 128K×4-bit RAM chips. How can you build a memory module of 1M×64-bit and how to connect this module with a computer system if the addressable unit is byte?

(Draw the address/data lines according to the example in the slides. It's fine to reuse the drawings in the slides as long as you get the address/data bus connection correctly labelled.)